

University of New Mexico
Department of Electrical and Computer Engineering

ECE 520 - VLSI Design (spring 2008)

Midterm Exam

Name: Answers

Date: March 26, 2008


Note: Only one 8½ inch by 11 inch page equation sheet, ruler, calculator, pencils, and pens are allowed.

1. (10 points) We have contacted a foundry to manufacture our VLSI test chip at 45nm technology. According to their device specs, the threshold voltage of NMOS is 0.30V when channel length $L=45\text{nm}$. However, when we simulate NMOS with $L=75\text{nm}$ in this technology, SPICE simulations show that the threshold voltage is 0.35V. Explain why?

This is due to threshold voltage roll-off.

 2. (20 points) Prior to CMOS technology, the logic gates were made of NMOS device only. The following circuit shows an inverter using NMOS only.
- (a) Assume that $V_T = 1V$, $K'_n = 100 \mu A/V^2$, $(W/L)_1 = (W/L)_2 = 10$, and $V_{DD} = 5V$. Find V_{OL} and V_{OH} of this inverter. Ignore body effect.
- (b) Write the expression for *input* and *output* parasitic capacitance of this inverter as a function of C_{OX} , C_J , C_{JSW} , A_D , P_D , C_{GDOV} , C_{GDOV} of M_1 and M_2 ?

$$a) \left\{ \begin{array}{l} V_{OH} = 4V \\ V_{OL} = 1.17V \end{array} \right.$$



$$b) C_{in} = C_{GDOV1} + C_{GSOV1} + W_1 C_{ox} L_{eff}$$

$$C_{out} = 2 C_{GDOV1} + K_{eq1} (C_{j1} A_{D1} + C_{jsw1} P_{D1}) + \frac{2}{3} W_2 C_{ox} L_{eff}$$

3. (30 points) For a MOSFET operating in the subthreshold regime ($V_{GS} < V_T$), the reduction in gate voltage needed to reduce the drain current by one decade is defined as the “subthreshold swing”, S , where


$$S = \frac{kT}{q} \ln(10) \left(1 + \frac{C_{Dep}}{C_{OX}} \right),$$

The unit of S is mV/decade.

- (a) Find S at room temperature for NMOS and PMOS devices. Assume that gate oxide thickness is $t_{OX} = 2 \text{ nm}$ for both NMOS and PMOS, and channel depletion depth in NMOS is $W_{Dep} = 30 \text{ nm}$ and in PMOS is $W_{Dep} = 15 \text{ nm}$ ($\epsilon_{SiO_2} = 3.9$ and $\epsilon_{Si} = 11.9$).
- (b) These devices are used in an inverter that operates in subthreshold region, where V_{DD} is less than device threshold voltages. Using the drain current equation at subthreshold region, calculate the leakage currents when the inverter input is set to 0 and 1 . The device measurements indicate that for the device sizes used in the inverter circuit, $I_{O(NMOS)} = 15 \mu\text{A}$ and $I_{O(PMOS)} = 10 \mu\text{A}$. Assume that $V_{DD} = 0.4\text{V}$, $V_{Tn} = |V_{Tp}| = 0.5\text{V}$ and $\lambda_n \approx \lambda_p \approx 0$.
- (c) Using the drain current equation at subthreshold region, compute the rise and fall propagation delays (50% delays) of the inverter, t_{PLH} and t_{PHL} . Assume that the total load capacitance of the inverter is 10 fF .

Hint: Drain current equation at subthreshold region is:
 
$$I_{DS} = I_0 e^{\frac{V_{GS} - V_T}{nKT/q}} \left(1 - e^{\frac{-V_{DS}}{KT/q}} \right) (1 + \lambda V_{DS})$$




a) $\left\{ \begin{array}{l} \text{NMOS: } S = 72 \text{ mV/dec} \\ \text{PMOS: } S = 84.2 \text{ mV/dec} \end{array} \right.$

b) $\left\{ \begin{array}{l} I_{DSn} = 1.645 \text{ pA} \\ I_{DSp} = 11.57 \text{ pA} \end{array} \right.$

This page is left blank to be used for problem 3

$$c) \left\{ \begin{array}{l} t_{PHL} = 3.28 \text{ ns} \\ t_{PLH} = 3.06 \text{ ns} \end{array} \right.$$

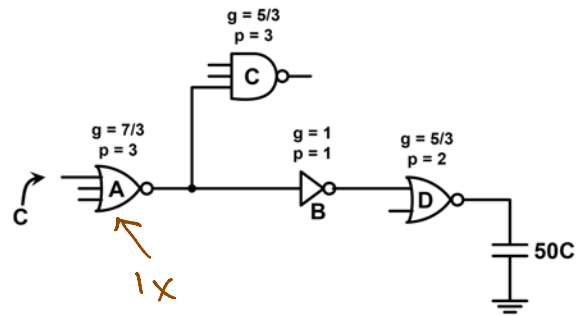4. (15 points) Use the logical effort technique in the circuit below.
- Find the minimum delay.
 - Optimize gate size for minimum delay.
 - Determine optimum transistor sizes for minimum delay.



a) $D_{min} = 30.1$ $C = 1 \times g_1 = \frac{7}{3}$

b) $C_{in}(D) = 10.37C$

$C_{in}(B) = 1.29C$

$C_{in}(A) = 1.0C$

c) $S_D = \frac{10.37 \times (\frac{7}{3})}{\frac{5}{3}} = 14.5X$

$S_B = \frac{1.29 \times (\frac{7}{3})}{1} = 3X$


$S_A = \frac{1 \times (\frac{7}{3})}{\frac{7}{3}} = 1X$

5. (15 points) Consider the following logic circuit that is used to implement function Z.
- What is the function Z? Explain how the circuit operates.
 - Although the circuit appears digitally correct, it operates slowly. Moreover, when two of these gates are cascaded, the results are unreliable. Suggest explanations for these two problems.
 - Propose a modification to the circuit which retains the general design but introduces two pairs of additional inverters to address the problems.

a) $Z = A \oplus B$

b) use of NMOS for Pullup and PMOS for Pull down.

 c) use of \bar{A} and \bar{B} when needed, instead.



6. (5 points) What is "Bent Gate"? What is the advantage and difficulty of using bent gate?

Bent Gate is a layout technique to reduce transistor area.

7. (5 points) What is STI? How does it help to scale CMOS technology?

shallow trench insulator.
It needs less space to isolate MOSFETs.